

The Inyo Force-Balance Vertical Seismometer

Circuit Description

Brett M. Nordgren
Rev. - 2 November, 2010

Introduction

The Inyo Force-Balance Broad Band vertical seismometer was designed to provide an excellent balance between cost/complexity and performance. Its mechanical design is relatively simple and rugged and can be duplicated by anyone who has some basic metalworking equipment and the skill to use it. The electronics are contained on a single PC board using a circuit which is adequate to give excellent performance, though no more complex than required.


The mechanical design uses an astatic spring configuration, but unlike the most elegant commercial instruments the spring is made from stainless steel rather than from an exotic low TC of Elasticity alloy. This means that the instrument response to the rate of temperature change will be perhaps 10x larger than the best sensors of equivalent bandwidth, but still quite reasonable. In addition, by removing a jumper, the output can be passed through a 1/125 Hz single-pole high-pass filter, which will hide essentially all temperature variation effects. In addition the design is such that it should not need to be mechanically re-balanced over its full operating temperature range.

The internal noise of the Inyo FBV is somewhat higher than the expensive commercial verticals, but in all but the quietest locations will not be seen above the seismic background. Side-by-side tests against a high quality instrument (Trillium Compact 120) show virtually identical waveforms, both when displaying seismic background signals as well as larger seismic events.

The mechanical elements are designed to be field-reparable, requiring only tools which can be obtained at any small hardware store. And all parts, mechanical and electronic are readily constructed or are available from on-line sources.

Circuit Overview

Following is an overview schematic which shows the major signal paths. The heavy black lines trace the forward, 'A', portion of the loop, starting at the capacitive position sensor and ending at the output of the feedback loop. The red lines trace the feedback branches of the loop, the 'B' path, starting at the loop output and ending at the force feedback coil. The blue lines trace the signal from where it exits the loop, through several alternative stages of amplification to the output terminals.

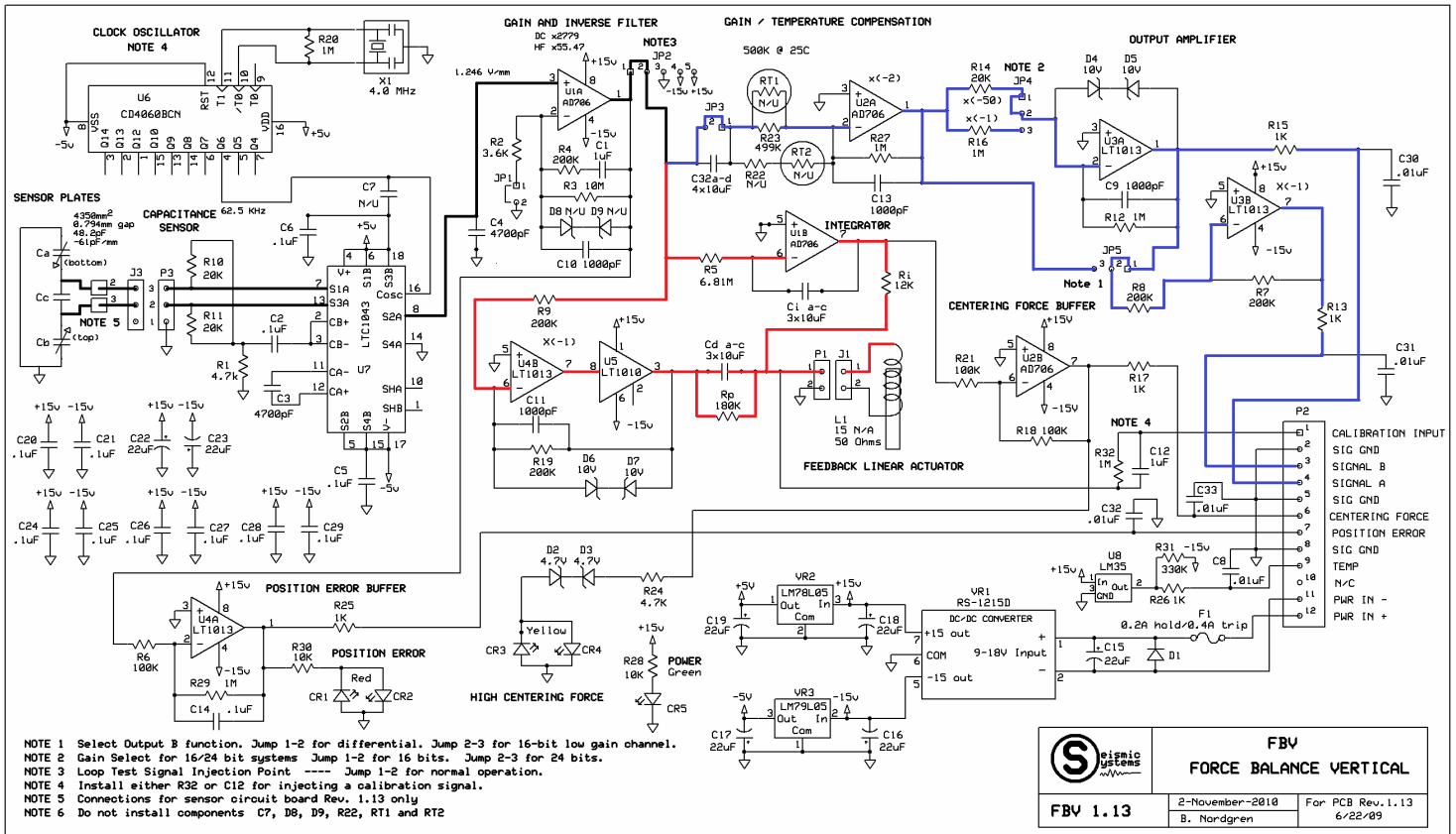

Capacitive Sensor

The capacitive sensor consists of two sensor plates, copper foil layers, on opposite sides of a stationary printed circuit board. Above and below the PC board are two moving, grounded plates which form capacitors C_a and C_b , and which change value as the moving plates change position. As the boom moves up, C_a increases in value while C_b decreases. The difference in capacitance is detected and amplified by U7 and its associated circuits. C_c is a stray capacitance of about 130 pF formed by the circuit board dielectric between the driven electrode plates of C_a and C_b .


The area of each capacitor plate is approximately 4350 mm² and when centered, their separation from the grounded plates is about 1/32" or 0.79mm, making the capacitance of each about 48.2 pF. As the boom moves a small distance from its rest position, the capacitor values change at a rate of 61pF/mm of motion, one increasing and one decreasing, though in practice, with feedback active, that motion will only be few micrometers or even less.

Although C_a , C_b , R10 and R11 may be viewed as a half-bridge circuit, they are more easily analyzed as a switched-capacitor, charge transfer problem. U7, via C2, R10 and R11, applies a 62.5kHz, 5V peak square wave to both C_a and C_b . Each half cycle of 8.0 μ s is sufficient to fully charge C_a and C_b . But if their values are slightly different, on the positive half cycle there will be a small difference in the charge transferred to each, and therefore a small net charge gets transferred to C3. On the negative half cycle a portion of that charge is transferred to output capacitor C4.

The result is that any unbalanced capacitance creates a voltage across the output capacitor of about 1.25V per mm of sensor motion. The 62.5kHz clock frequency and the capacitor values used, result in a transfer function pole having a time constant of about 0.52ms, representing a frequency roll off at 306 Hz.


External Clock

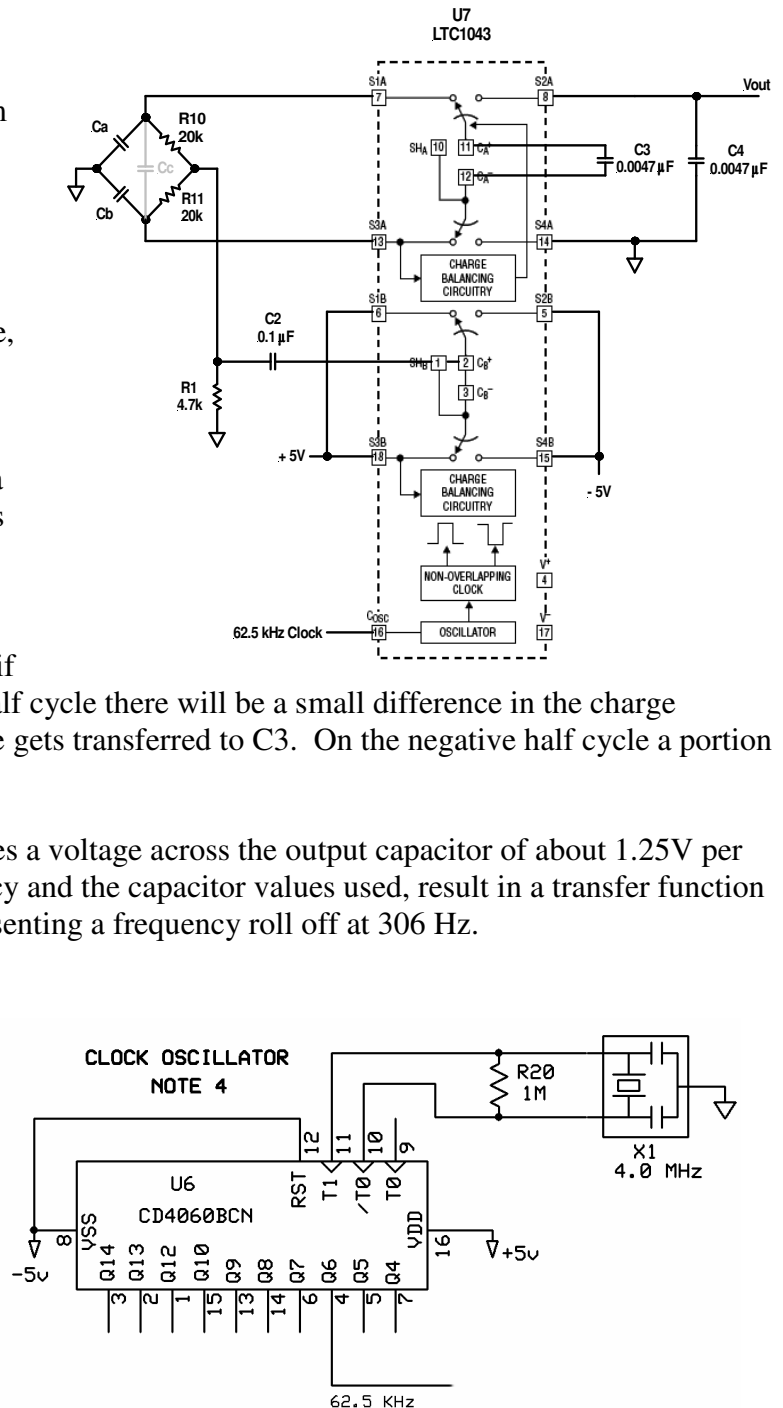Since the gain of the sensor circuit is proportional to frequency it is desirable to maintain close control of the clock frequency. Therefore provision was made to install a higher stability clock in place of the LTC1043 internal oscillator. The clock is obtained by dividing down a 4MHz ceramic resonator to obtain the 62.5kHz signal.



Gain and Inverse Filter

Amplifier U1A provides the remainder of the gain in the forward-directed portion of the feedback loop. This is a frequency-shaped, high-stability amplifier, providing a gain of 55.5 at all frequencies of interest, with an additional gain at DC of 50.1, making the DC gain equal to 2779. At a frequency of about 0.016 Hz the gain begins to fall, leveling out again at about 0.8 Hz. This frequency characteristic has been called the 'inverse filter' and it is designed to compensate for the loss of loop gain at the low end of the instrument operating band due to the falling velocity response of the spring portion of the spring-mass, with decreasing frequency. Diodes D8 and D9 are not currently being installed.

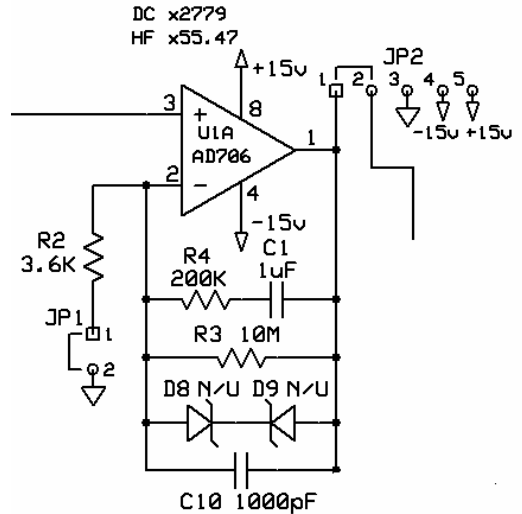


Jumper JP1 may be removed to reduce the amplifier gain to 1 for testing and adjustment purposes.

Jumper JP2 is used to provide an insertion point for a test signal, applied in such a way that the loop can still remain active. After removing the 1-2 jumper a plug can be installed on JP2 to connect and power a test adapter which consists mainly of an instrumentation amplifier.

Derivative Inverter-Buffer

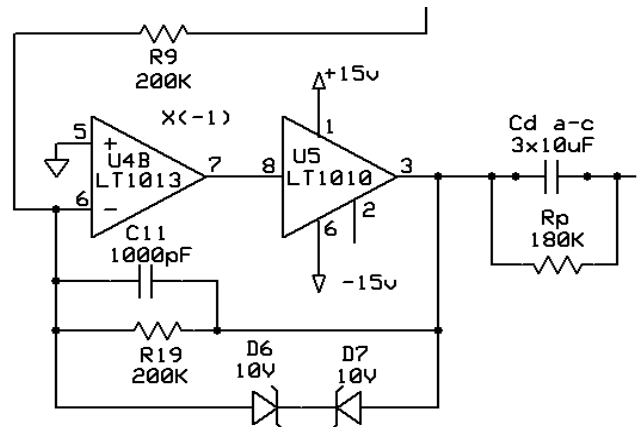
In order to match the signal polarity of the integrator, the signal to the Derivative and Proportional branches is inverted by U4B and U5. Buffer U5 is needed in order to properly drive the derivative capacitor C_d in series with L1, the Feedback Linear Actuator coil, which, at 50Hz represent a combined load impedance of 117 ohms—too low to be directly driven by an ordinary op-amp output.



Integrator

The integral feedback branch is constructed using a feedback integrator circuit built around a high-stability amplifier.

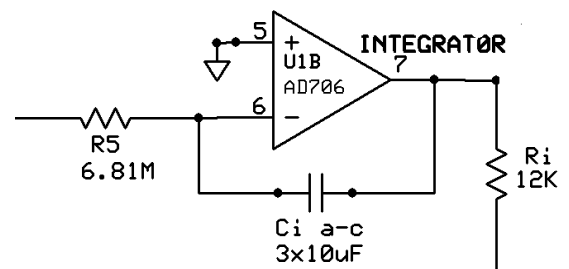R_i , the integral scaling resistor determines the relative strength of the integral feedback. It also represents a limit on how much unbalance force the integrator can handle, and it is designed to be able to compensate for the force change of the steel spring over the expected operating temperature range.



Output Amplifier Gain Following Loop					
Mode	JP4	JP5	Signal A	Signal B	Differential
16-bit	1-2	2-3	100.2	2.004	---
16-bit differential	1-2	1-2	100.2	-100.2	200.4
24-bit	2-3	2-3	2.004	2.004	---
24-bit differential	2-3	1-2	2.004	-2.004	4.008

Instrument Generator Constant V / m/s					
Mode	JP4	JP5	Signal A	Signal B	Differential
16-bit	1-2	2-3	75,150	1,503	---
16-bit differential	1-2	1-2	75,150	-75,150	150,300
24-bit	2-3	2-3	1,503	1,503	---
24-bit differential	2-3	1-2	1,503	-1,503	3,006

Peak clipping Velocity for given digitizer clipping voltage - m/s					
Mode	JP4	JP5	Signal A	Signal B	Differential
16-bit	1-2	2-3	1.3307E-04	6.6534E-03	---
16-bit differential	1-2	1-2	---	---	1.3307E-04
24-bit	2-3	2-3	6.6534E-03	6.6534E-03	---
24-bit differential	2-3	1-2	---	---	6.6534E-03

Power Supply

The power supply uses a voltage regulated DC/DC converter, VR1, to provide DC isolation from the external power source, whose voltage may vary over a range which includes the voltage range of a 12V lead-acid battery. The converter provides supply voltages of + and - 15 Volts, which are also regulated by regulators VR2 and VR3 down to + and - 5 Volts for those circuits which require the lower, better regulated voltages.

Input protection is provided by resettable PTC device, F1, which has a nominal operating current rating of 0.2A and a trip rating of 0.4A. Diode D1 protects against reversed polarity conditions. Normal input current draw is approximately 60 mA.

